

# EX#2-Sequential Synthesis and FPGA Programming

Ali Ghahari 810100201

Mohammad Sadeghi 810100175

**Introduction:** In this experience, we will design an Multi-channel Synchronous Serial communication Demultiplexer(MSSD) which see the Huffman coding style , simulation and synthesis through it.

## A) RTL Design

In this module we get *serin* input after that *start* signal change from 1 to 0. The first two bit of *serin* indicate the port number (*p*) which output transmit on it. The 4 next bit stands for bit number of data (*n*) and *n* last bit is data value. at the end *done* signal become 1 when *start* return to 1.

 


Fig1

The circuit component show in fig2 and we will explain:

- 1) We need *one\_pulser* to create a *clk* pulse during button push.
- 2) Two *data\_counter* and *port\_counter* to calculate the port detecting clock cycles and data count numbers.
- 3) Two shift register for saving the port number and data bit number.
- 4) Demux for selecting the choosen port to transsmmit the output.
- 5) A Controller unit to manage the module states.
- 6) Seven segment display for showing the entered bit of data.

By giving each bit of data the number of seven segment decrease until reach zero. also for each bit of *serin* we must push button so *one\_puser* can create a single clock.

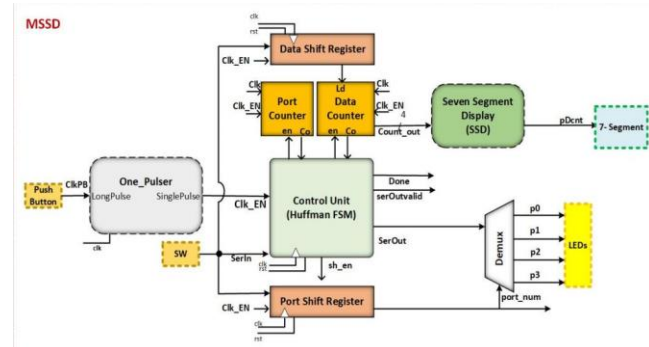



Fig2

## One\_pulser


We will see verilog code of module and simulateion waveform:

```
1 |
2 | module OnePulser(clkpb , clk , rst , clken);
3 | input clkpb , clk , rst;
4 | output clken;
5 |
6 | parameter A = 2'b00 , B = 2'b01 , C = 2'b10;
7 |
8 | reg [1:0]ps;
9 | reg [1:0]ns;
10 |
11 | always @(posedge clk , posedge rst) begin
12 |     if(rst)
13 |         ps = A;
14 |     else
15 |         ps = ns;
16 | end
17 |
18 | assign clken = ps == B;
19 | AliGhAliGh, 6 days ago • init
20 | always @(ps , clkpb) begin
21 |     ns = A;
22 |     case (ps)
23 |         A: ns = clkpb ? B : A;
24 |         B: ns = C;
25 |         C: ns = clkpb ? C : A;
26 |         default: ns = 2'bxx;
27 |     endcase
28 | end
29 |
30 | endmodule
```

 This one pulser has state diagram with 3 states. when we push button clkpb become 1 and we go to B state and from there we go to C unconditionally. we stay at last state until clkpb toggle to 0 and then go back to first state.




So we have simulate result in wave:

 

We can see during clkpb become 1 we have clk pulse in output.
 
## FSM controller

First let see the state diagram for MMSD controller:



Let list the input signals:

- 1) Serin: main input which read bit by bit
- 2) co1&co2: carry out of two counter which count two for port number and four for datanumber

- 3) cod: its for loadcounter which become 0 when we send all bit of data.
- 4) Clk,rst,clken: synchronous controll signals

Now output of state machine:

- 1) Cnt1&cnt2 : these signals allow counters of datapath to start counting.
- 2) Cntd : do as well for load counter.
- 3) Ldcounter: this signal will initialize the seven\_segment number for show as data bit number and with each bit we have read this number decrease by loadcounter.
- 4) Shen & shend : allow shift\_registers to receive and save data.
- 5) Valid: identify that we are reading valid bit data for data value.
- 6) Done : it is signal for ensure that process get end.

```

1 module Controller(clk,clken,rst,serin,co1,co2,cod,cnt1,cnt2,cntd,ldcntd,shen,shend,valid,done);
2 input serin,co1,co2,cod,clk,rst,clken;
3 output cnt1,cnt2,cntd,ldcntd,shen,shend,valid,done;
4
5 parameter IDLE = 3'b000, PORT = 3'b001, NUM = 3'b010, DATA = 3'b011, DONE = 3'b100, LDC = 3'b101;
6
7 reg[2:0] ns,ps;
8
9 always @(posedge clk,posedge rst) begin
10     if(rst)
11         ps = IDLE;
12     else if(clken) ps = ns;
13 end
14
15 assign done = ps == DONE;
16 assign cnt1 = ps == PORT;
17 assign cnt2 = ps == NUM;
18 assign cntd = ps == DATA;
19 assign ldcntd = ps == LDC;
20 assign shen = ps == PORT;
21 assign shend = ps == NUM;
22 assign valid = (ps == DATA) || (ps == LDC);
23
24 always @(serin,co1,co2,cod,ps) begin
25     ns = 3'bxxx;
26     case (ps)
27         IDLE: ns = serin ? IDLE : PORT;
28         PORT: ns = co1 ? NUM : PORT;
29         NUM: ns = co2 ? LDC : NUM;
30         DATA: ns = cod ? DONE : DATA;
31         DONE: ns = serin ? IDLE : PORT;
32         LDC: ns = DATA;
33         default: ns = 3'bxxx;
34     endcase
35 end
36 endmodule

```

## Counters

We have counter code with 2bit state which pass it the load value as parameter. What that means?

For example when load set to 0, the counter count four and go back to 0;

And for two count we set load to 2;

This is verilog of counter:

```
module Counter #(parameter load) (clk ,rst ,clken ,cnt ,co);
    input clk ,rst ,clken ,cnt;
    output co;

    reg[1:0] ps;

    always @(posedge clk, posedge rst) begin
        if(rst)
            ps = load;
        else if(clken && cnt)
            ps = ps + 1;
        end

    assign co = ps == 2'b11;
endmodule
```

As you see, when we reach to state 3 the cout become one.

Exactly, we are counting one unit less.

But however we must read one bit to go to next state so it is no matter.

But the load counter dose not have parameter:

```
module LdCounter (clk ,rst ,clken ,data ,cnt ,ld ,co ,out);
    input clk ,rst ,clken ,cnt ,ld;
    input[3:0] data;
    output co;
    output reg[3:0] out;

    always @(posedge clk, posedge rst) begin
        if(rst)
            out = 0;
        else if(ld && clken)
            out = data - 1;
        else if(clken && cnt)
            out = out - 1;
        end

    assign co = out == 1;
endmodule
```

In this counter we have the data number in first and with each bit that we have receive during clkpb we decrease the number of counter output which say to seven\_segment its value to show.

## The Demux

This component will select that which port should data go on it.

The selector have input and 4 port as output that select one of them from value of port register to send input on that port.

```
module Demux(serin, port ,p0 ,p1 ,p2 ,p3);
    input serin;
    input[1:0] port;
    output p0 ,p1 ,p2 ,p3;

    assign p0 = port == 0 ? serin : 1'b0;
    assign p1 = port == 1 ? serin : 1'b0;
    assign p2 = port == 2 ? serin : 1'b0;
    assign p3 = port == 3 ? serin : 1'b0;
endmodule
```

## Shift\_Registers

There is no complex thing with this part. we receive bits and set them in register from left (means if we send 1,0,0,0 in order register final value will be 0001)

```
1 module ShReg #(parameter n)(serin ,en ,rst ,clk ,clken ,out);
2 input serin ,en ,rst ,clk ,clken;
3 output reg[n-1:0] out;
4
5 always @(posedge clk, posedge rst) begin
6     if(rst)
7         out = 0;
8     else if(clken && en)
9         out = {out ,serin};
10 end
11 endmodule
```

the port number register must be 2 bit and data num register must be 4 so we use parameter method in verilog code.



## Seven segment

In last component we have SSD which can show us 0 to 15 in hex based on input it gets:

```
1 module SSD(inp ,out);
2 input[3:0] inp;
3 output reg[6:0] out;
4
5 parameter _0 = 7'h40;
6 parameter _1 = 7'h79;
7 parameter _2 = 7'h24;
8 parameter _3 = 7'h30;
9 parameter _4 = 7'h19;
10 parameter _5 = 7'h12;
11 parameter _6 = 7'h02;
12 parameter _7 = 7'h78;
13 parameter _8 = 7'h00;
14 parameter _9 = 7'h10;
15 parameter _a = 7'h08;
16 parameter _b = 7'h03;
17 parameter _c = 7'h46;
18 parameter _d = 7'h21;
19 parameter _e = 7'h06;
20 parameter _f = 7'h0e;
21
22 always @(inp) begin
23     out = 0;
24     case (inp)
25         0: out = _0;
26         1: out = _1;
27         2: out = _2;
28         3: out = _3;
29         4: out = _4;
30         5: out = _5;
31         6: out = _6;
32         7: out = _7;
33         8: out = _8;
34         9: out = _9;
35         10: out = _a;
36         11: out = _b;
37         12: out = _c;
38         13: out = _d;
39         14: out = _e;
40         15: out = _f;
41         default: out = 7'bx;
42     endcase
43 end
44 endmodule
```

According to fig-1 in page 1 this SSD has 4bit input that represent data bit number and set 7 bit output which is value of seven\_segment circuit.

## MMSD Implementation


First of all we wiring all components and also controller unit in main module:

```
module MMSD(serin, clkpb, clk, rst, p0, p1, p2, p3, done, valid, sevseg);
    input serin, clkpb, clk, rst;
    output p0, p1, p2, p3, done, valid;
    output[6:0] sevseg;

    wire clken, col, cod, cnt1, cnt2, cntd, ldcntd, shen, shend, valid, done;
    wire[1:0] port;
    wire[3:0] segdata, dnsout;

    OnePulser OP(.clkpb(clkpb), .clk(clk), .rst(rst), .clken(clken));
    Controller C(.clk(clk), .clken(clken), .rst(rst), .serin(serin), .col(col), .co2(co2), .cod(cod), .cnt1(cnt1), .cnt2(cnt2), .cntd(cntd),
    .ldcntd(ldcntd), .shen(shen), .shend(shend), .valid(valid), .done(done));
    Counter #2 PC(.clk(clk), .rst(rst), .clken(clken), .cnt(cnt1), .co(co1));
    Counter #4 DMC(.clk(clk), .rst(rst), .clken(clken), .cnt(cnt2), .co(co2));
    Demux DM(.serin(serin), .port(port), .p0(p0), .p1(p1), .p2(p2), .p3(p3));
    LDCounter LC(.clk(clk), .rst(rst), .clken(clken), .data(dnsout), .cnt(cntd), .ld(ldcntd), .co(cod), .out(segdata));
    ShReg #2 PMS(.serin(serin), .en(shen), .rst(rst), .clk(clk), .clken(clken), .out(port));
    ShReg #4 DNS(.serin(serin), .en(shend), .rst(rst), .clk(clk), .clken(clken), .out(dnsout));
    SSD_ssd(.inp(segdata), .out(sevseg));
endmodule
```

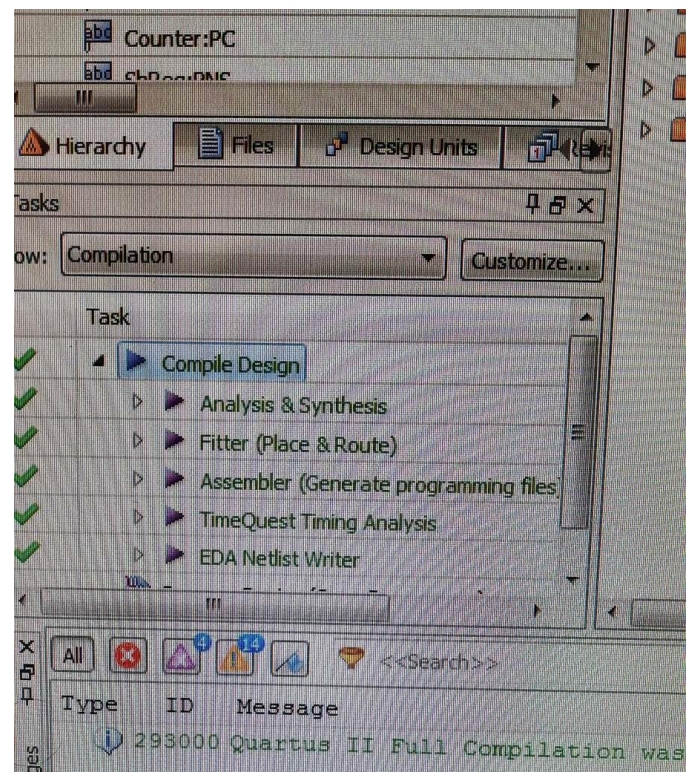Now we convey these codes on new wizard project which we create in Quartus 12.1 and before synthesis we should compiled all files:




As we can see analysis and synthesis, routing and prepost synthesis sections done well without error (just some warnings)


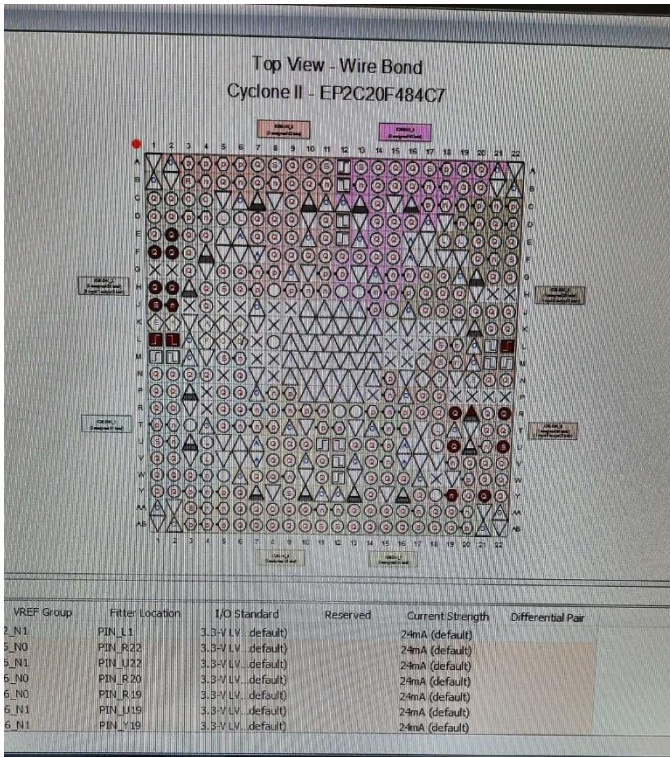
## Pin assignment

At next part as we use cyclone II for this project we must set our input map with circuit pin which its informations are available in manuall.

We get input(*serin,rst,clkpb*) from board buttons and see outputs(*port,done,valid*) on LEDs and data numbers on seven\_segment:



The pins assign in bellow way:

- 1) Four red LED pins for port number
- 2) One switch pin for *rst*
- 3) One switch pin for *serin*
- 4) One button pin for *clkpb*
- 5) Two green LED pin for *done* and *valid* signal.
- 6) Default pins for seven\_segment

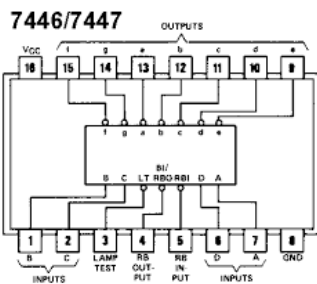


Fig3-SSD pins

## Observation

At last by running synthesisable version of code on board we saw the result and went through this procedure:

- 1) Set *rst* to 1 for resetting all things
- 2) Set *serin* as 0 to start.
- 3) Set two serial 1 to set port 3.
- 4) Set two 0 and two 1 again to set data number 3 (means 3 bit)
- 5) By giving first bit of data *valid* LED turn on but *seven\_segment* isn't active yet because it is in LDC state in controller.
- 6) By sending next bit *seven\_segment* begin count down from 2 (because one bit of data already recieved)
- 7) At last when *seven\_segment* reach to 0 we send 1 in *serin* again and waiting for *rst* because in this implementation the counter don't have internal restart signal

Here is one shot from our final circuit when SSD begin to count down (data num was 6):

